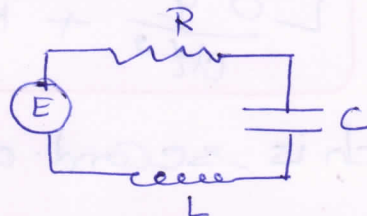


Note Application of D.E to LRC-circuit

①

→ Here we will consider the application of ~~Kirchhoff's~~ D.E to series circuit containing 1) electromotive force 2) resistor 3) Inductor + 4) Capacitor

→ Electromotive force (eg battery or generator) produces a flow of current in a closed circuit + this current produces so called voltage drop across each resistor, inductor + Capacitor



→ Fundamental laws in the theory of electric circuits

Kirchhoff's voltage law →

The algebraic sum of instantaneous voltage drop ~~across resistor, inductor~~ around a close circuit in a specific direction is zero.

OR

The sum of the voltage drop across inductor, resistor + Capacitor is equal to total electromotive force (emf) in a closed circuit

→ Mathematically

$$L \frac{di}{dt} + Ri + \frac{1}{C} q = E \quad \text{--- (1)}$$

Voltage drop across Inductor

Voltage drop across resistor

Voltage drop across Capacitor

$L \rightarrow$ inductance
 $R \rightarrow$ Resistance
 $C \rightarrow$ Capacitance

So we have

$$L \frac{di}{dt} + Ri + \frac{1}{C} q = E \quad \text{--- (1)}$$

$\because i = \frac{dq}{dt}$ --- (2) So Put it in (1)

$$L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = E \quad \text{--- (3)}$$

which is second order non homogeneous linear D.E in (2)

Again, diff (1) w.r.t (t)

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = \frac{dE}{dt} \quad \text{--- (4)}$$

which is 2nd order NHDE (linear) in (i).

* As per Q asked we can use either (3) or (4).

Note \rightarrow The 2nd order linear NHDE reduces to 1st order in two cases \rightarrow

1) If circuit has no capacitor \rightarrow

From eqn (1)

$$L \frac{di}{dt} + Ri = E$$

2) If circuit has no inductor \rightarrow

From (1)

$$Ri + \frac{1}{C} q = E$$

\Rightarrow

$$R \frac{dq}{dt} + \frac{1}{C} q = E$$

eg ① A circuit has in series an emf given by $E = \sin t$ volt, resistor of 2Ω , inductor of $1H$.
 If initial current is zero. Find current at any time $t > 0$. ③

Soln → ∴ the D.E governing the current in LRC-circuit is given by →

$$L \frac{di}{dt} + Ri + \frac{1}{C} q = E \quad \text{--- (1)}$$

∴ there is no capacitor so (1) reduces to

$$L \frac{di}{dt} + Ri = E \quad \text{--- (2)}$$

$$\frac{di}{dt} + 2i = \sin t \quad \text{--- (3)}$$

$\Omega = \text{ohm}$
 $H = \text{henry}$
 ~~\times~~

So I.F = $e^{\int 2 dt} = e^{2t}$ } ④

So G.S of (3) is →

$$i(e^{2t}) = \int (\sin t) e^{2t} dt + C$$

$$i(e^{2t}) = \frac{e^{2t}}{5} (2\sin t - \cos t) + C \quad \leftarrow (\text{solving})$$

⑤

∴ given that at $t=0$, $i=0$.

$$\text{So } 0 = \frac{1}{5}(-1) + C \Rightarrow \boxed{C = \frac{1}{5}}$$

So (5) becomes —

$$i(e^{2t}) = \frac{1}{5} e^{2t} (2\sin t - \cos t) + \frac{1}{5}$$

$$\boxed{i = \frac{1}{5} (2\sin t - \cos t) + \frac{1}{5} e^{-2t}}$$

→ Desired Soln.

eg (2)

A circuit has in series an emf given by $\cos t$ V, resistor of 3Ω , inductor of 1 H and capacitor of 0.5 farad. If initial current + charge on capacitor are zero. Find charge on capacitor at any time $t > 0$. (4)

Soln \rightarrow \because current at any time ($t > 0$) in LRC circuit is governed by D.E \rightarrow

$$L \frac{di}{dt} + Ri + \frac{1}{C} q = E \quad \text{--- (1)}$$

So as per given Q, (1) changes to

$$\frac{di}{dt} + 3i + 2q = \cos t \quad \text{--- (2)}$$

\because we have to find charge at any $t > 0$ on capacitor so

using $i = \frac{dq}{dt}$ in (2) we get

$$\frac{d^2 q}{dt^2} + 3 \frac{dq}{dt} + 2q = \cos t \quad \text{--- (3)}$$

which is linear NHDE in (3).

$$\text{HDE} \rightarrow \frac{d^2 q}{dt^2} + 3 \frac{dq}{dt} + 2q = 0 \quad \text{--- (4)}$$

$$\text{A.E} \rightarrow m^2 + 3m + 2 = 0$$

$$\text{Roots} \rightarrow m = -1, -2.$$

$$\text{G.S of HDE (4) is} \rightarrow \left[q_g = C_1 e^{-t} + C_2 e^{-2t} \right] \quad \text{--- (5)}$$

Now for finding ~~particular~~ particular

Soln of (3) we can either use M.O.V.C
OR M.O.V.P.

let us use $\text{MOVC} \rightarrow$

5

$$\text{So } q_p = A \cos t + B \sin t \quad \left(\begin{array}{l} \text{0.0} \quad \text{2(t)} \\ \quad \quad = \cos t \\ \quad \quad \times \text{ (3)} \end{array} \right) \quad \text{--- (6)}$$

$$\text{So } q_p' = -A \sin t + B \cos t \quad \text{--- (7)}$$

$$q_p'' = -A \cos t - B \sin t \quad \text{--- (8)}$$

So put $q_p, q_p' + q_p''$ in (3) we get \rightarrow

$$(-A \cos t - B \sin t) + 3(-A \sin t + B \cos t) + 2(A \cos t + B \sin t) = \cos t$$

$$\cos t (A + 3B) + \sin t (B - 3A) = \cos t + 0 \cdot \sin t$$

Comparing coefficients of ~~cos t~~ & sin t we get

$$\left. \begin{array}{l} A + 3B = 1 \\ -3A + B = 0 \end{array} \right\} \text{Solving we get} \rightarrow \left. \begin{array}{l} A = \frac{1}{10} \\ B = \frac{3}{10} \end{array} \right\}$$

$$\text{So } q_p = \frac{1}{10} \cos t + \frac{3}{10} \sin t \quad \text{--- (9)}$$

Hence G.S of D.E (3) is

$$= q_g + q_p$$

$$= (C e^{-t} + D e^{-2t}) + \frac{1}{10} \cos t + \frac{3}{10} \sin t$$

RLC - Circuits (Application of D.E)

Q1 An emf $E = 200e^{-5t}$ is applied to a series circuit consisting of 20 ohm resistor + 0.01 F capacitor. Find Charge + current at any time assuming that there is no initial charge on capacitor.

Q2 Find current in a series circuit with $R = 10 \Omega$, $L = 2 H$
 $E(t) = 20 \cos t$. Determine current at any time $t \geq 0$

Q3 A circuit consist of an inductance of 2 Henry, resistance of 4 ohm + capacitance of 0.05 farad. If the charge + current is initially zero then find charge at any time
(+) if there is constant emf of 100 volts.

Soln

① $q = 10te^{-5t}$ $i = 10e^{-5t} - 50te^{-5t}$	② $i(t) = \cos 5t + \sin 5t - e^{-5t}$	③ $q(t) = 5 + \frac{5}{3}e^{-\frac{t}{3}} (3\cos 3t + \sin 3t)$
--	--	---